



Voltage Rating of Capacitor C3 is  $V_o * 2 = 5V * 2 = 10V$

### 3. Output Diode D3

Since the output rectifier diode turns on and off at the switching frequency, it uses a fast recovery diode that can switch at high speed (66kHz or above).

The reverse voltage applied to the output diode should be less than or equal to the margin:

$$V_{dr} = \frac{VIN_{max}}{0.7} = \frac{264 * 1.41}{0.7} = \frac{372}{0.7} = 531V \Rightarrow \text{select } 600V \text{ products}$$

Diode losses are approximate, but are:

$$P_d = V_F * I_{out} = 1V * 0.17A = 0.17W$$

$V_F$  means diode's forward voltage.

### 4. $R_{BIAS}$ (R4) and $R_{FB}$ (R2)

The value of  $R_{BIAS}$ (R4) and  $R_{FB}$  (R2) are selected such that, at the regulated output voltage, the voltage on the FEEDBACK pin ( $V_{FB}$ ) is 2.0V. This voltage is specified for a FEEDBACK pin current ( $I_{FB}$ ) of 49uA.

Let the value of  $R_{BIAS}$ (R4) = 2.49 kOhm; this bias the feedback network at amount of ~0.8mA

Hence the value of  $R_{FB}$  (R2) is given by

$$\begin{aligned} R_{FB} &= \frac{V_o - V_{FB}}{\frac{V_{FB}}{R_{BIAS}} + I_{FB}} = \frac{(V_o - V_{FB}) * R_{BIAS}}{V_{FB} + (I_{FB} * R_{BIAS})} \\ &= \frac{(5VDC - 2VDC) * 2.49kOhm}{2V + (49uA * 2.49kOhm)} \\ &= 3520.25 Ohm \Rightarrow 3.48 kOhm \end{aligned}$$

### 5. Verification

$$\text{solve} \left( \frac{(x - 2) \cdot 2490}{2 + (49 \cdot 10^{-6} \cdot 2490)} = 3480, x \right)$$

$$x = 4.9657 \text{ VDC}$$

## Part III: Circuit Implementation