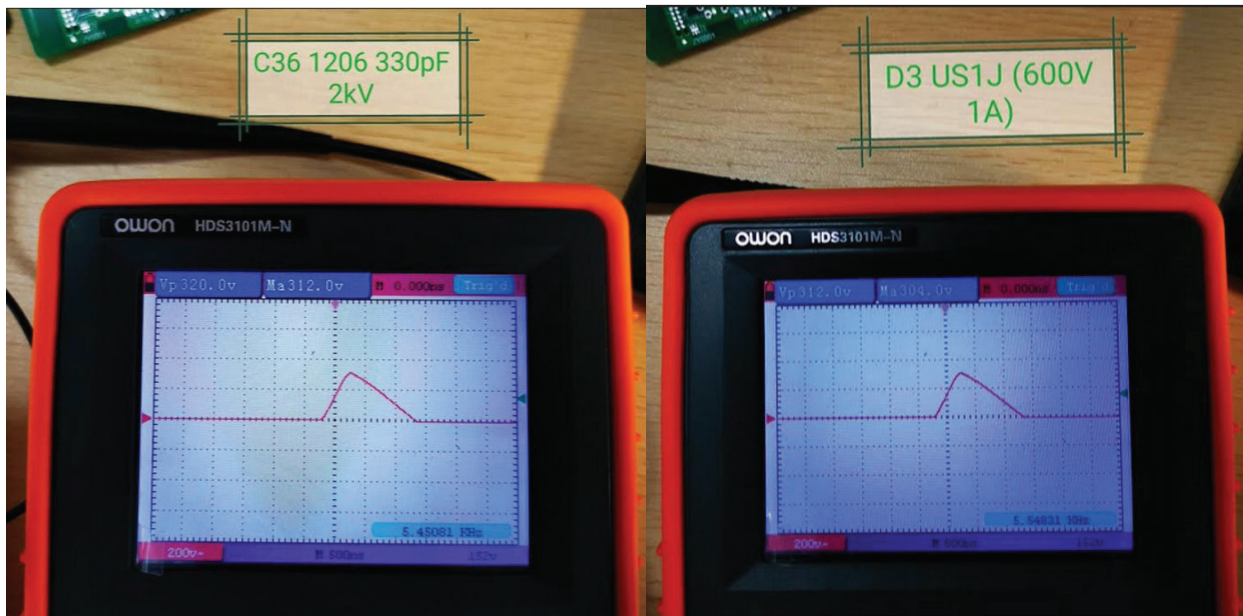
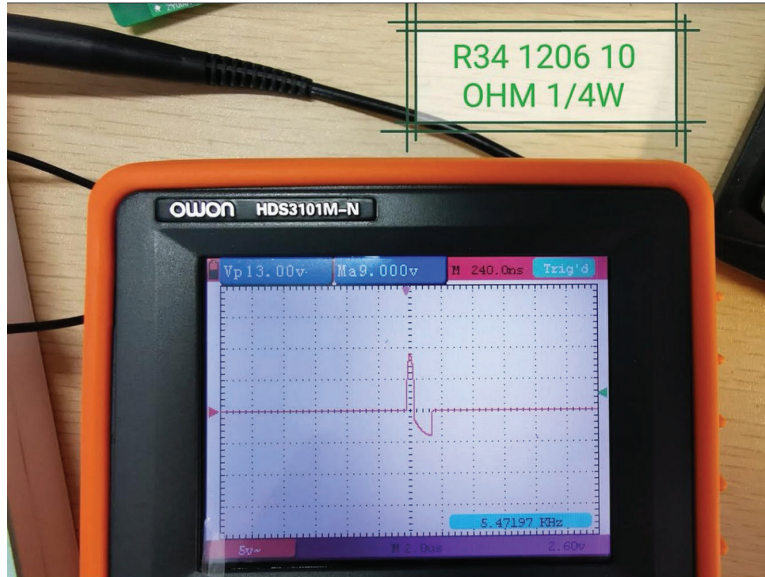




C4, C5 and L1 are PI filter for EMI suppression. R34 and C36 in parallel to D3 are used to reduce spikes occurring ON/OFF.

Some measurement results when the input was 220VAC, 50Hz:



Part IV: Mean Time To Failure (MTTF) and Thermal Analysis

Test Contents: