



This design has excellent performance in theory, but it is impossible to manufacture 178 Ohm transmission line for almost all widely used substrates. Due to the limitations in manufacturing, the cascading solution should be used for this Matching Structure.

We know that the RX Impedance of MMIC is  $Z_{RX} = 104.667 + 38.391j$  Ohm @ 24GHz. The first stage (TL10), transforms the impedance from  $104.667 + 38.391j$  Ohm to  $60 - 25j$  Ohms. The final stage (TL11), transforms the impedance from  $60 - 25j$  Ohms to 50 Ohms.

