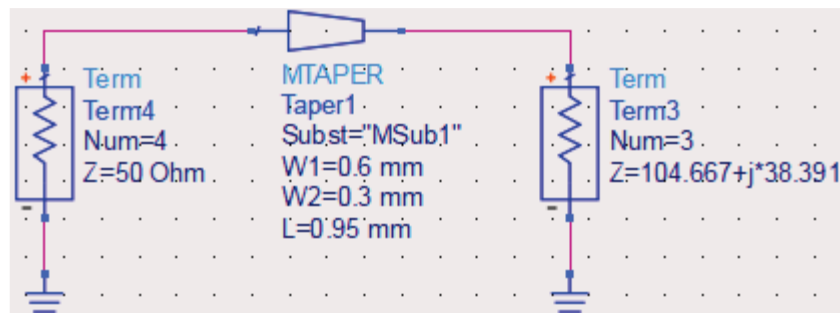





Components of the RX Matching Structures will be discussed in the following sections.

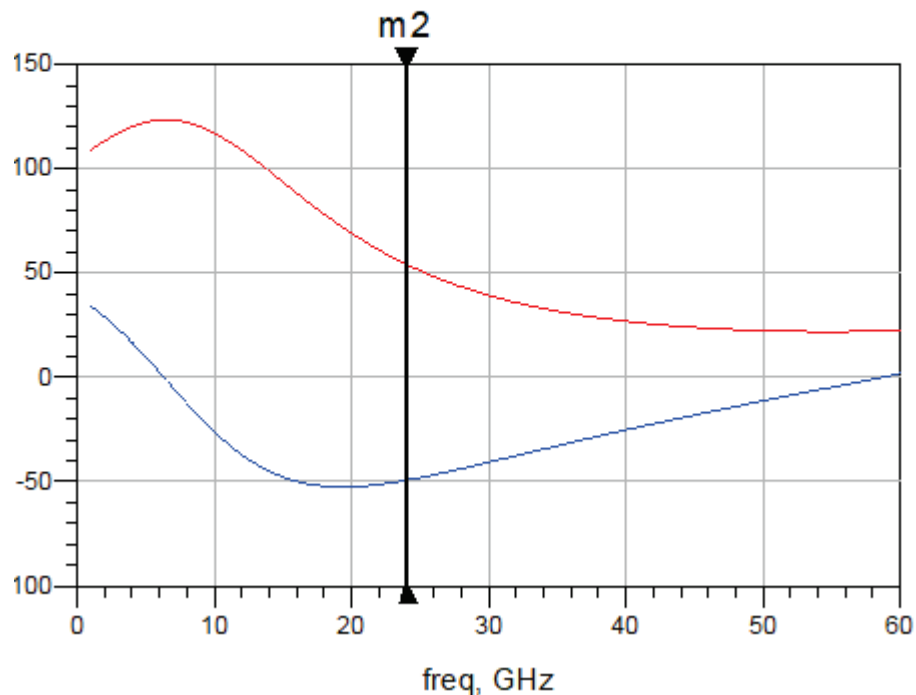a. Tapered Transformer

By tapering a transmission line, a very broadband impedance match (low VSWR) can be realized over a wide bandwidth, the longer the taper, the wider the frequency band [2].



m2
freq=24.00GHz
real(Zin4)=54.180
imag(Zin4)=-49.294



The tapered transformer transformed the impedance from $Z_{RX} = 104.667 + 38.391j$ Ohm to $54.18 - 49.294j$ Ohm.

b. Stepped Impedance Filter

In this application, this filter is mainly used to match the Tapered Transformer's output impedance $54.18 - 49.294j$ Ohm to 50 Ohm.