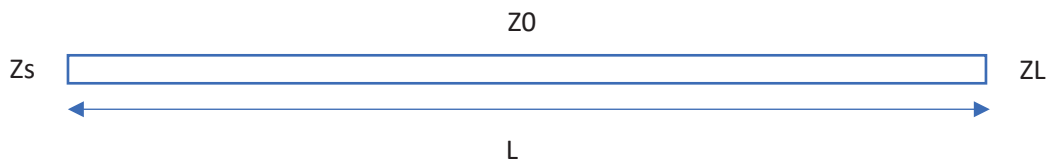




Appendix A

- Transmission Line Matching Technology-

Infineon’s Official Evaluation Board used Stepped Impedance Filter for impedance matching. Stepped Impedance Filter can be used to match the impedance within the relatively small PCB footprint. However, the design process is not straightforward enough. Transmission Line Matching Technology can be used to solve the impedance matching problem straightforwardly within the relatively larger PCB footprint.



For a transmission line with characteristic impedance Z_0 , load Z_L and length L .

$$Z_S = Z_0 \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \tag{1}$$

Plug $Z_s = R_s + jX_s$ and $Z_L = R_L + jX_L$ into the equation (1) and we also know that the transmission line length $\theta = \beta l$:

$$Z_0 = \sqrt{\frac{R_s |Z_L|^2 - R_L |Z_s|^2}{R_L - R_s}} \tag{2}$$

$$\theta = \arctan\left(\frac{Z_0(R_s - R_L)}{R_s X_L + R_L X_s}\right) \tag{3}$$

For BGT24LTR11N16, the tapered transformer transformed the impedance from $Z_{RX} = 104.667 + 38.391j$ Ohm to $54.18 - 49.294j$ Ohm. We are going to match the impedance from $54.18 - 49.294j$ Ohm to 50 Ohm.

We know that $R_s = 54.18$ Ohm, $X_s = -49.294$ Ohm, $R_L = 50$ Ohm, $X_L = 0$ Ohm. So that $Z_s = 54.18 - 49.294j$ Ohm and $Z_L = 50$ Ohm

Thus, according to equations (2) and (3):

$$Z_0 = 178.2547917 \text{ Ohm}$$

$$\theta = 16.82062539 \text{ degrees}$$

